

## **Multiplexers in Digital Logic**


**It is a combinational circuit which have many data inputs and single output depending on control or select inputs**

**for  $2^n$  input lines,  $n$  selection lines are required.**


**Multiplexers are also known as  $n$  selector, parallel to serial convertor, many to one circuit, universal logic circuit**

**Multiplexer can act as universal combinational circuit. All the standard logic gates can be implemented with multiplexers.**

## Logic Circuit Of 2-To-1 Multiplexer

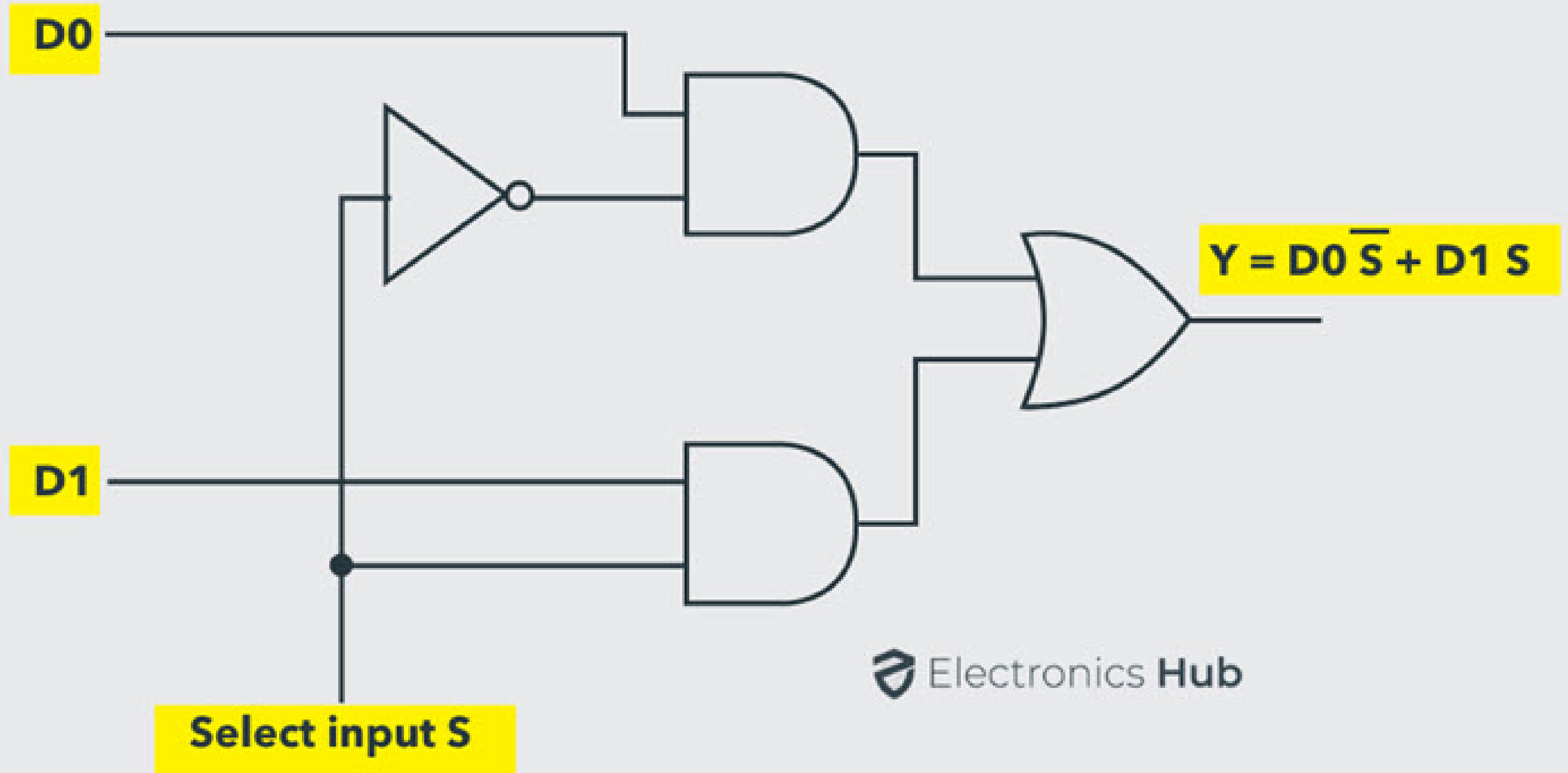

## 4 to 1 multiplexer

 

## Truth Table

S0	S1	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

So, final equation,

$$Y = S0'.S1'.I0 + S0'.S1.I1 + S0.S1'.I2 + S0.S1.I3$$


 


Fig. 1: 4x1 Multiplexer
 
# Implementation of NOT gate using 2 : 1 Mux



Truth Table


x	f
0	1
1	0

We can analyze it

$$Y = x'.1 + x.0 = x'$$

It is NOT Gate using 2:1 MUX.

 
# Implementation of AND gate using 2 : 1 Mux



Truth Table

x	y	f	$f \rightarrow y$
0	0	0	f = 0
0	1	0	
1	0	0	f = y
1	1	1	
 
# Implementation of OR gate using 2 : 1 Mux




Truth Table

$x$	$y$	$f$	$f \rightarrow y$
0	0	0	$f = y$
0	1	1	
1	0	1	$f = 1$
1	1	1	


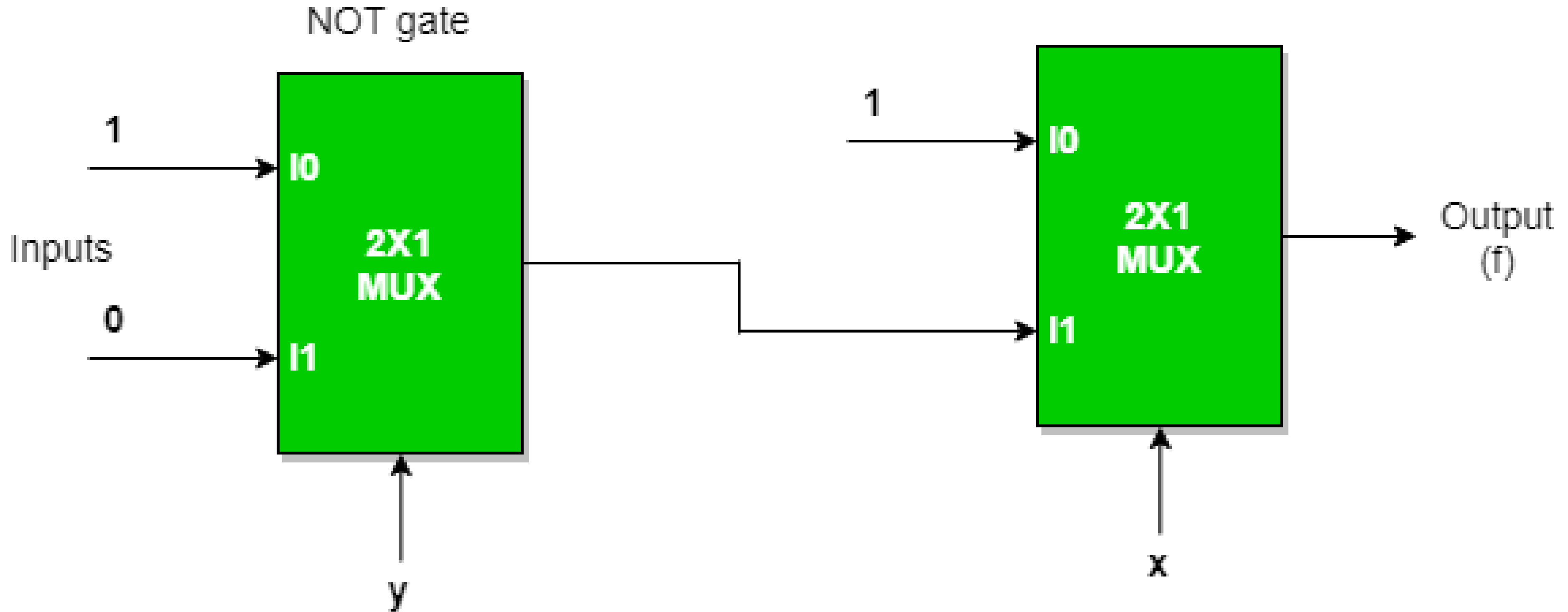
# Implementation of NAND gate using 2 : 1 Mux




# **nand gate using 4 to 1 multiplexer**


# xor gate using multiplexer

**xnor gate using 4 to 1 multiplexer**


# Demultiplexers

 **A demultiplexer, sometimes abbreviated dmux, is a circuit that has one input and more than one output. It is used when a circuit intends to send a signal to one of many devices.**



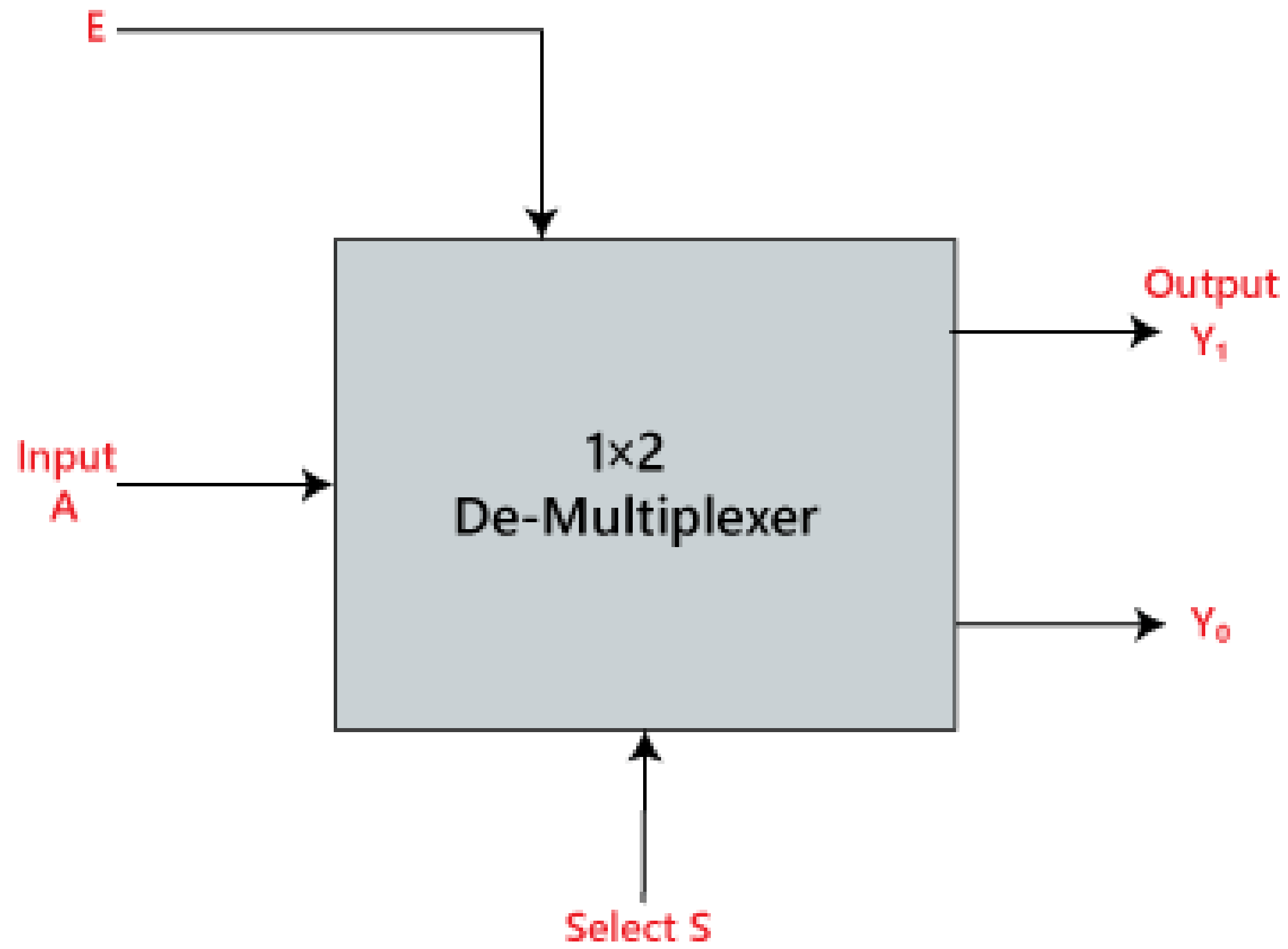

INPUTS		Output	
$S_0$		$Y_1$	$Y_0$
0		0	A
1		A	0

 

**The logical expression of  
the term  $Y$  is as follows:**

$$Y_0 = S_0'.A$$


$$Y_1 = S_0.A$$
 
## **1×4 De-multiplexer:**

In 1 to 4 De-multiplexer, there are total of four outputs, i.e., Y0, Y1, Y2, and Y3, 2 selection lines, i.e., S0 and S1 and single input, i.e., A.

On the basis of the combination of inputs which are present at the selection lines S0 and S1, the input be connected to one of the outputs.





INPUTS		Output			
$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	A
0	1	0	0	A	0
1	0	0	A	0	0
1	1	A	0	0	0

**The logical expression of the term Y is as follows:**

$$Y_0 = S_1' S_0' A$$

$$y_1 = S_1' S_0 A$$

$$y_2 = S_1 S_0' A$$

$$y_3 = S_1 S_0 A$$

